

## فصل ۳

دانش فنی، اصول، قواعد، قوانین و مقررات

**Definition of  $i$**

The number  $i$  is such that  $i = \sqrt{-1}$

Imaginary Unit

$\sqrt{-1} = i$        $\sqrt{-b} = i\sqrt{b}$


$(\sqrt{-1})^2 = i^2$        $\sqrt{-16} = i\sqrt{16} = 4i$

$-1 = i^2$

**Complex Numbers**

$a + bi$

Real Part      Imaginary Part

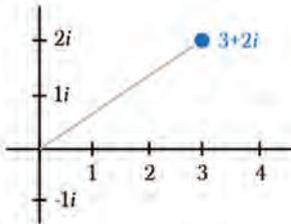

$a + bi$

Where  $i = \sqrt{-1}$

and if  $i = \sqrt{-1}$


then  $i^2 = -1$

90° rotation:  $i^1 = \sqrt{-1} = +i$

180° rotation:  $i^2 = (\sqrt{-1})^2 = -1$

270° rotation:  $i^3 = (\sqrt{-1})^3 = -i$

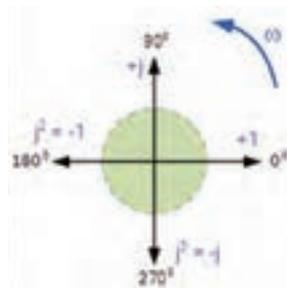360° rotation:  $i^4 = (\sqrt{-1})^4 = +1$



**Adding Complex Numbers**

$(3+3i) + (5-2i)$

$= (8)$

Firsts      Lasts

$(a+bi)(c+di)$

Outers      Inners

$(3+2i)(-4) = -12i - 8i^2$

$= -12i - 8(\sqrt{-1})^2$

$= -12i - 8(-1)$

$= -12i + 8$

$(8+7i) + (4+3i)$       Like Terms

Like Terms       $= (8 + 4) + (7i + 3i)$

$= \boxed{12 + 10i}$

$i = \sqrt{-1}$

$7x + 3x = 10x$

## Complex impedances

Back to the index.

With the next calculator, several properties are calculated for a series circuit build with a resistor and a coil or capacitor.

Enter the frequency, resistor and coil / capacitor value in the yellow coloured fields, and click on “calculate”.

Frequency:	<input type="text"/>	MHz	
Resistor value:	<input type="text"/>	$\Omega$	
In series with:	<input type="text"/>	$\mu F$ (capacitor) *	
	<input type="button" value="Calculate"/>	<input type="button" value="Reset"/>	
Complex impedance	<input type="text"/>	$\Omega$	<a href="#">More info</a>
Q factor	<input type="text"/>		<a href="#">More info</a>
Absolute impedance	<input type="text"/>	$\Omega$	<a href="#">More info</a>
Phase between current and voltage	<input type="text"/>	degrees	<a href="#">More info</a>
Parallel resistor	<input type="text"/>	$\Omega$	<a href="#">More info</a>
Parallel impedance	<input type="text"/>	$\Omega$ . This corresponds to <input type="text"/>	

This way of describing the impedance is however not complete, because the phase between voltage and current is not shown.

From the value X, we can't see if it is a resistor, coil or capacitor.

## Complex impedance

A complex impedance is build up with a real part ( $R$ =resistor) in series with a imaginary part ( $+jX$  = coil or  $-jX$  = capacitor).

A complex impedance is indicated with the the letter  $Z$ , and the unit is  $\Omega$ .

The notation of a complex impedance can be  $Z = R + jX$ .

In this case a resistor and coil are series connected.

The impedance of the coil is:  $X = 2 \cdot \pi \cdot F \cdot L$

With a coil, the (alternating) voltage will always run  $90^\circ$  ahead of the current, this is indicated with  $+j$ .

The notation for complex impedance can also be:  $Z=R-JX$ .

In this case a resistor and capacitor are series connected.

The impedance of the capacitor is  $X = (1/2\pi FC)$

With a capacitor, the (alternating) voltage will always run  $90^\circ$  behind the current, this is indicated with the -J.

**Example 1**

$$Z1 = 220 + J300 \Omega$$

In this example a resistor of  $220 \Omega$  and a coil with a impedance of  $300 \Omega$  are series connected.

These two components in serie make one complex impedance.

**Example 2**

$$Z2 = 470 - J80 \Omega$$

In this example a resistor of  $470 \Omega$  and a capacitor with an impedance of  $80 \Omega$  are series connected.

**Example 3**

$$Z3 = 100 + J0 \Omega$$

This is a pure resistor of  $100 \Omega$  (at that frequency).

Because the imaginary part is zero, we can also write :  $Z3=100-J0 \Omega$

**Example 4**

$$Z4 = 0 + J60 \Omega$$

This is a coil with a impedance of  $60 \text{ Ohm}$ , this coil has no series resistance.

**Example 5**

$$Z5 = 0 - J400 \Omega$$

This is a capacitor with an impedance of  $400 \Omega$ , this capacitor has no series resistance.

**The J operator**

The letter J in complex impedances is called the J operator.

In a resistor the voltage across the resistor and the current through it are in phase, there is no phase difference.

The impedance of a resistor is called a real impedance.

The impedance of a coil is not real but imaginary.

In a coil, the voltage always runs  $90^\circ$  ahead of the current, this is indicated by +J followed by the impedance value.

A capacitor is also a imaginary impedance.

In a capacitor the voltage runs always  $90^\circ$  behind the current, this is indicated with -J followed by the impedance value.

## Calculating with the J operator

If we are calculating with imaginary impedances, the following rules apply:

$$J = \sqrt{-1}$$
$$1/-J = J$$

$$J^2 = -1$$
$$Ja + Jb = J(a+b)$$

$$1/J = -J$$
$$J-a = -Ja$$

## Adding complex impedances

If two complex impedances are series connected, a new complex impedance is formed. When adding two complex impedances, we can add the real parts, and also add the imaginary parts.

Example:  $Z_1$  and  $Z_2$  are series connected, the sum of these two is  $Z_6$ .

$$Z_1 = 220 + J300 \ \Omega$$

$$Z_2 = 470 - J80 \ \Omega \quad +$$

$$Z_6 = 690 + J220 \ \Omega$$

The imaginary parts are added, but because the imaginary part of  $Z_2$  is negative, it is in fact subtracted from the imaginary part of  $Z_1$ .

Another example:  $Z_7 = Z_1 + Z_2 + Z_3 + Z_4 + Z_5$

$$Z_1 = 220 + J300 \ \Omega \quad +$$

$$Z_2 = 470 - J80 \ \Omega \quad +$$

$$Z_3 = 100 + J0 \ \Omega \quad +$$

$$Z_4 = 0 + J60 \ \Omega \quad +$$

$$Z_5 = 0 - J400 \ \Omega$$

---

$$Z_7 = 790 - J120 \ \Omega$$

The sum of all these impedances behaves on that frequency the same as a resistor of  $790 \ \Omega$  is series with a capacitor with  $120 \ \Omega$  impedance.

## Resonance

If a capacitor and coil are series connected, and the imaginary parts are equal, they will add to zero  $\Omega$ .

The circuit then is in series resonance, and only the resistance of both components is left.

In series resonance, the impedance of the LC circuit will reach the lowest value.

With parallel LC circuits, the impedance will reach the highest value at resonance.

## The Q factor

We can calculate the quality factor (Q) of a complex impedance.

The Q ratio between imaginary part and real part of the impedance.

$$Q=X/R$$

It doesn't matter if the imaginary part is positive or negative, in the calculation we only use the number behind the J.

The Q has no unit, and the value is always positive (or zero, in case of a pure resistor).

Example:  $Z_7=790-J120 \Omega$  has an Q of 0.1519

### The absolute value of the impedance

If we connect an alternating voltage to the complex impedance, a current will flow. To calculate the value of the current, we need to know the absolute value of the impedance. The absolute value is indicated with  $|Z|$  and the unit is  $\Omega$ .

For an complex impedance  $Z=R\pm jX$  is the absolute value:

$$|Z| = \sqrt{(R^2 + X^2)}$$

Example:  $Z_7 = 790 - j120 \Omega$

$$|Z_7| = \sqrt{(790^2 + 120^2)} = 799 \Omega$$

If this impedance is connected to alternating voltage, a current will flow with the value:

$$I = U / |Z|$$

Example: the voltage across  $Z_7$  is 10 Volt RMS.

$$|Z_7| = 799 \text{ Ohm}$$

$$I = 10 / 799 = 0.0125 \text{ Ampere RMS.}$$

### Phase between voltage and current

The phase between the voltage across the complex impedance and the current through it can be calculated as follows:

Phase = arctangens ( $\pm X/R$ ).

The unit is degrees ( $^\circ$ )

The X value can be both positive or negative, according to the sign before the J operator.

With a positive value for phase, voltage runs ahead of the current.

With a negative value for phase, voltage runs behind the current.

The value for phase can vary from  $+90^\circ$  (coil), via  $0^\circ$  (resistor) to  $-90^\circ$  (capacitor).


### Example

With a complex impedance of  $Z_7=790-J120 \Omega$  the phase between voltage and current is:


$$\text{Phase} = \text{arctangens} (-120 / 790) = -8.6^\circ$$
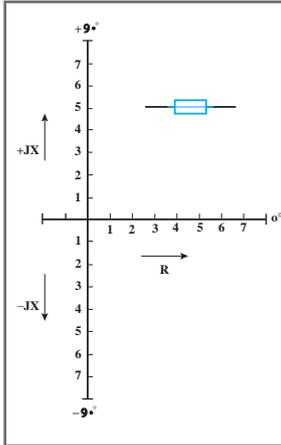
## Impedances as vectors


Complex impedances can be placed as vectors into a diagram. The angle with the horizontal axis indicates the phase between voltage and current, the length of the vector corresponds to the value of the impedance.




**A resistor of  $4 \Omega$**

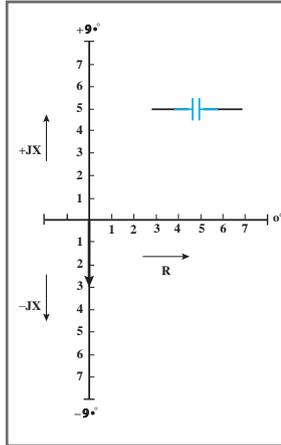

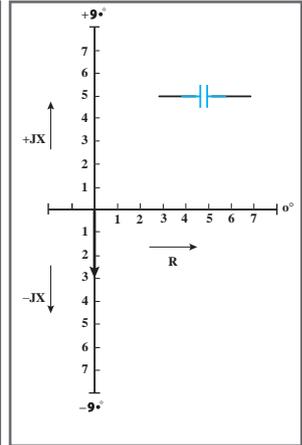**A coil with complex impedance  $+j3 \Omega$**



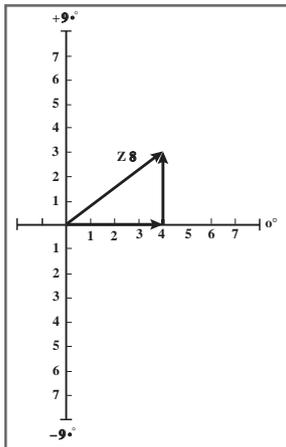**A capacitor with complex impedance  $-j5 \Omega$**




**A complex impedance:  $Z8=4+j3 \Omega$**

**The length of vector  $Z8$  is equal to the absolute value  $|Z8|$ .**


**In this case:  $|Z8| = \sqrt{(4^2 + 3^2)} = 5 \Omega$**
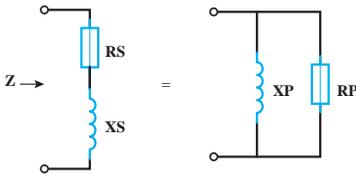
## Converting series impedance to parallel impedance

A complex impedance consisting of a resistor in series with a coil / capacitor can be converted into a parallel circuit of a resistor and a coil / capacitor. Both circuits will behave completely the same on that frequency, but this is only true for one frequency at which we calculate the circuit.



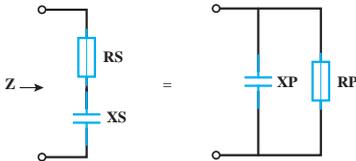A series circuit of resistor and coils converted into a parallel circuit of resistor and coil.



A series circuit of resistor and capacitor is converted into a parallel circuit of resistor and capacitor.

The conversion works as follows:

We have the complex series circuit  $Z = R_S + jX_S$

$R_S$  and  $X_S$  are the series components

With the next formulas we can find the values for the parallel components  $R_P$  and  $X_P$

$$R_P = (R_S^2 + X_S^2) / R_S$$

$$X_P = j(R_S^2 + X_S^2) / X_S$$

When the complex impedance is capacitive, so  $Z = R_S - jX_S$  then also the value of  $X_P$  will be negative.

### Example 1

The complex impedance is  $Z = 20 + j15 \Omega$

The parallel impedances are:

$$R_P = (20^2 + 15^2) / 20 = 31.25 \Omega$$

$$X_P = j(20^2 + 15^2) / 15 = +j41.67 \Omega$$

A series circuit of resistor and coil is converted into a parallel circuit of resistor and coil

### Example 2

The same component values, but now for a capacitive impedance

The complex impedance is  $Z = 20 - j15 \Omega$

The parallel impedances are:

$$R_P = (20^2 + (-15)^2) / 20 = 31.25 \Omega$$

$$X_P = j(20^2 + (-15)^2) / -15 = -j41.67 \Omega$$

A series circuit of resistor and capacitor is converted into a parallel circuit of resistor and capacitor.